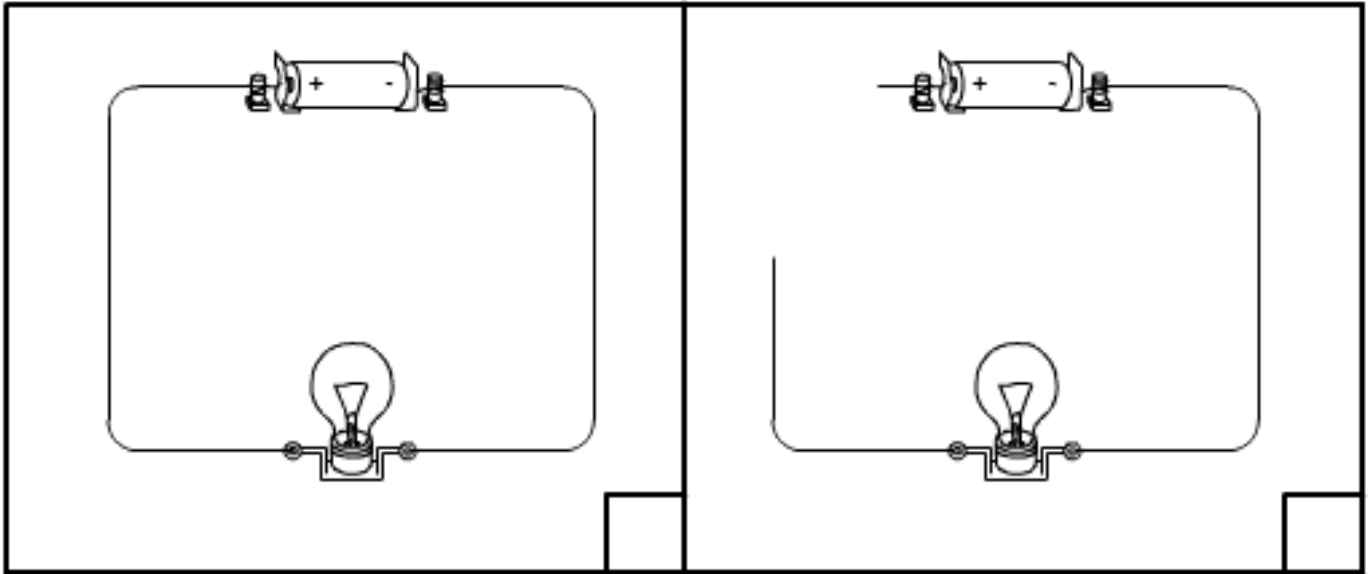


L.O. To know how components should be set out to create a simple circuit.

Using electricity

Name.....

Look at each circuit below. If you think the bulb will light, colour the bulb yellow and put a tick in the box. If you do not think the bulb will light, put a cross in the box.



Will this bulb light up? _____

Why? _____

Will this bulb light up? _____

Why? _____

bulb

wire

battery

electricity

circuit

connect